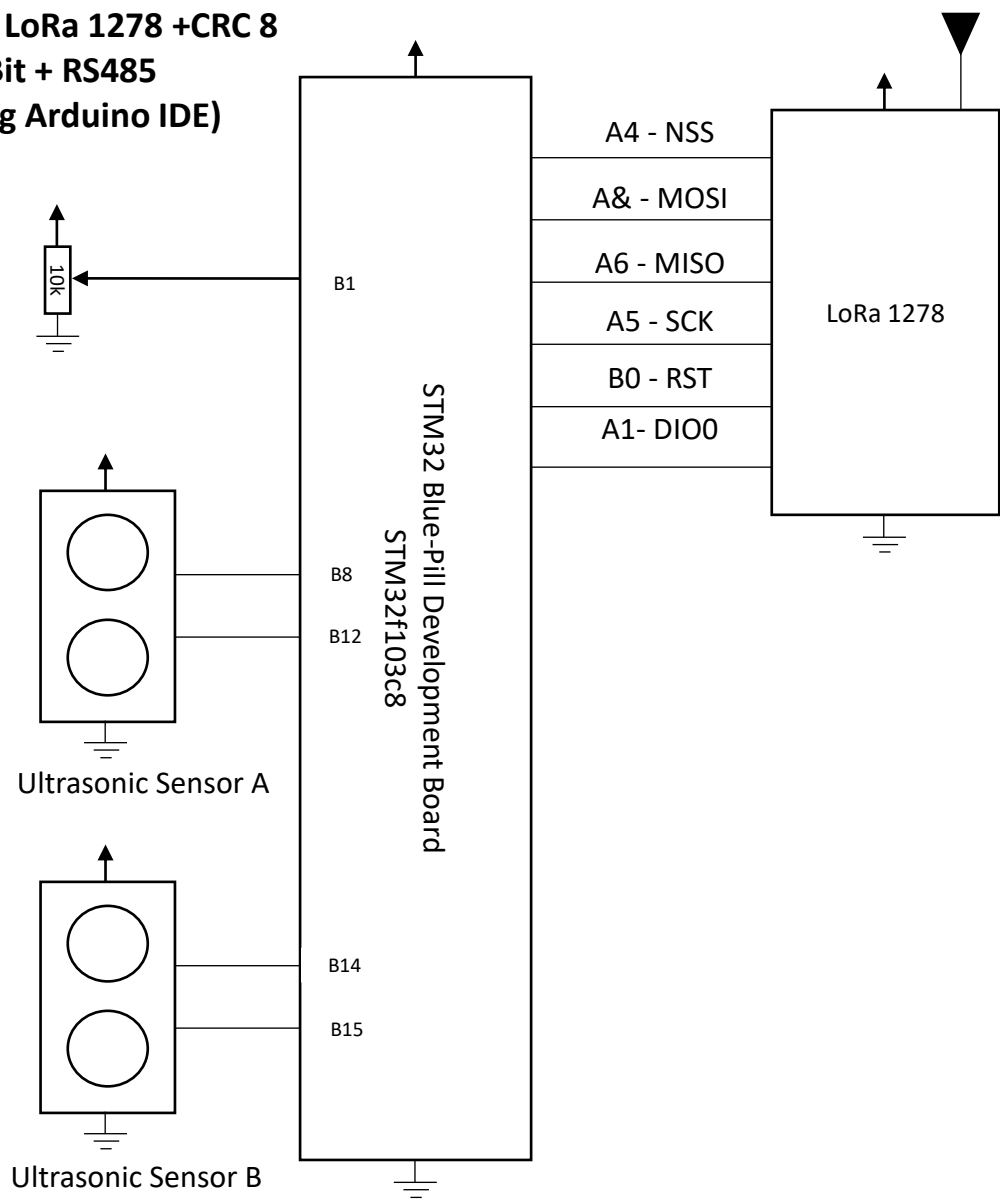



STM32 + LoRa 1278 +CRC 8
Bit + RS485
(Using Arduino IDE)



Tx Circuit Diagram
(Careful about the voltage of each component)

Antenna

Antenna

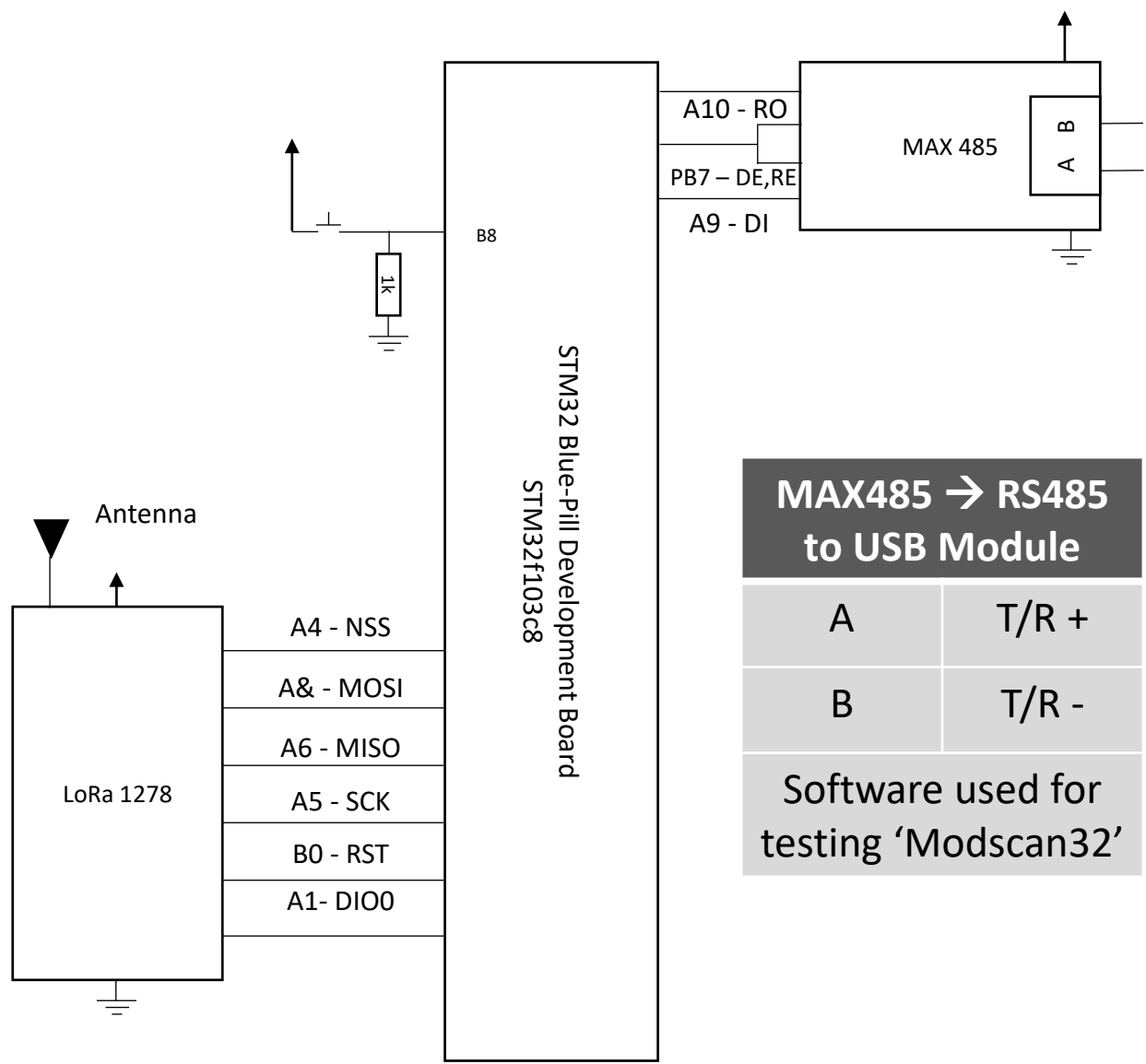

Rx Circuit Diagram
(Careful about the voltage of each component)

**MAX485 → RS485
to USB Module**

A	T/R +
B	T/R -

Software used for
testing 'Modscan32'